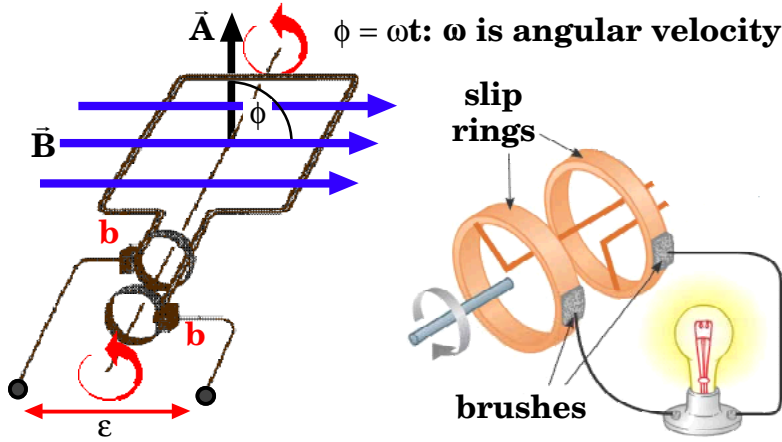


## CHAPTER 29

### ALTERNATING CURRENT CIRCUITS

- ac generators
- Resistance in ac circuits and rms values
  - † *Introduction to phasors*
- Inductors in ac circuits
- Capacitors in ac circuits
- *R-C-L circuits with an ac generator*
  - † *Resonance and tuned circuits*



$\vec{A}$   $\phi = \omega t$ :  $\omega$  is angular velocity


$\vec{B}$

slip rings

brushes

$\epsilon$

**Flux through coil:**
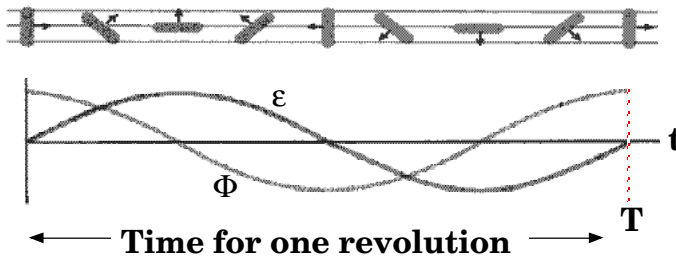
$$\Phi = \vec{B} \cdot \vec{A} = BA \cos \phi = BA \cos(\omega t).$$
$$\therefore \frac{d\Phi}{dt} = -\omega BA \sin(\omega t).$$
$$\therefore \epsilon = -\frac{d\Phi}{dt} = \omega BA \sin(\omega t).$$


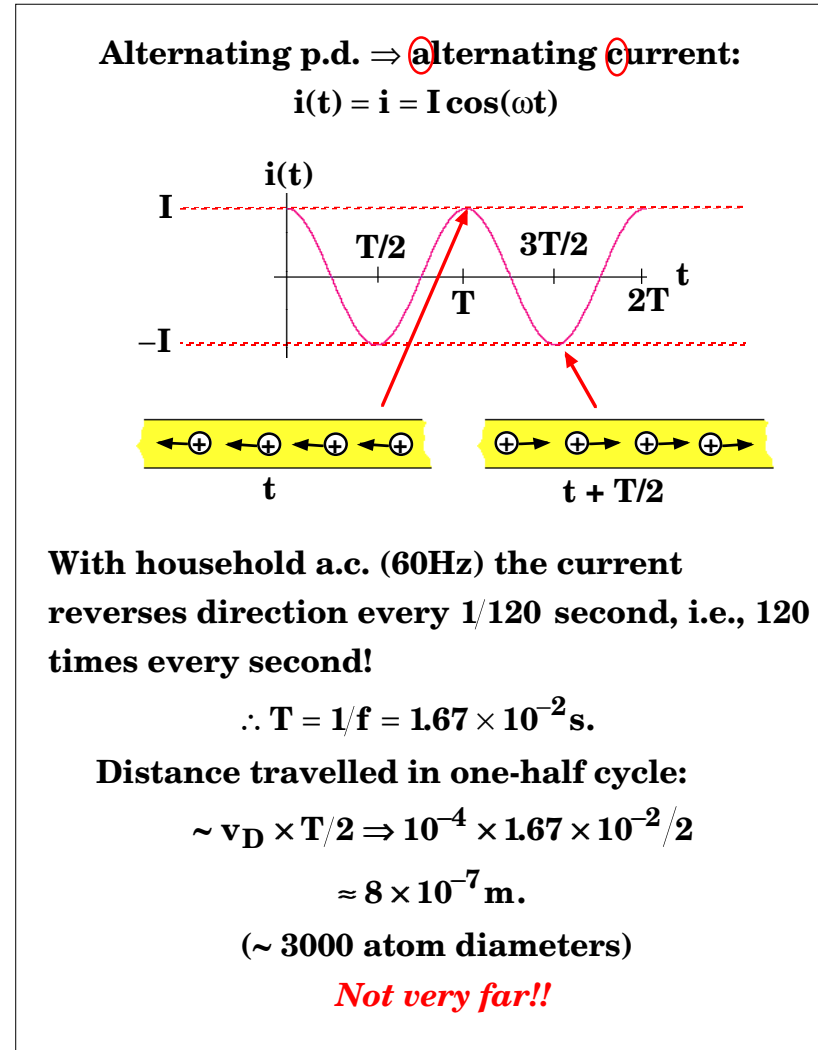
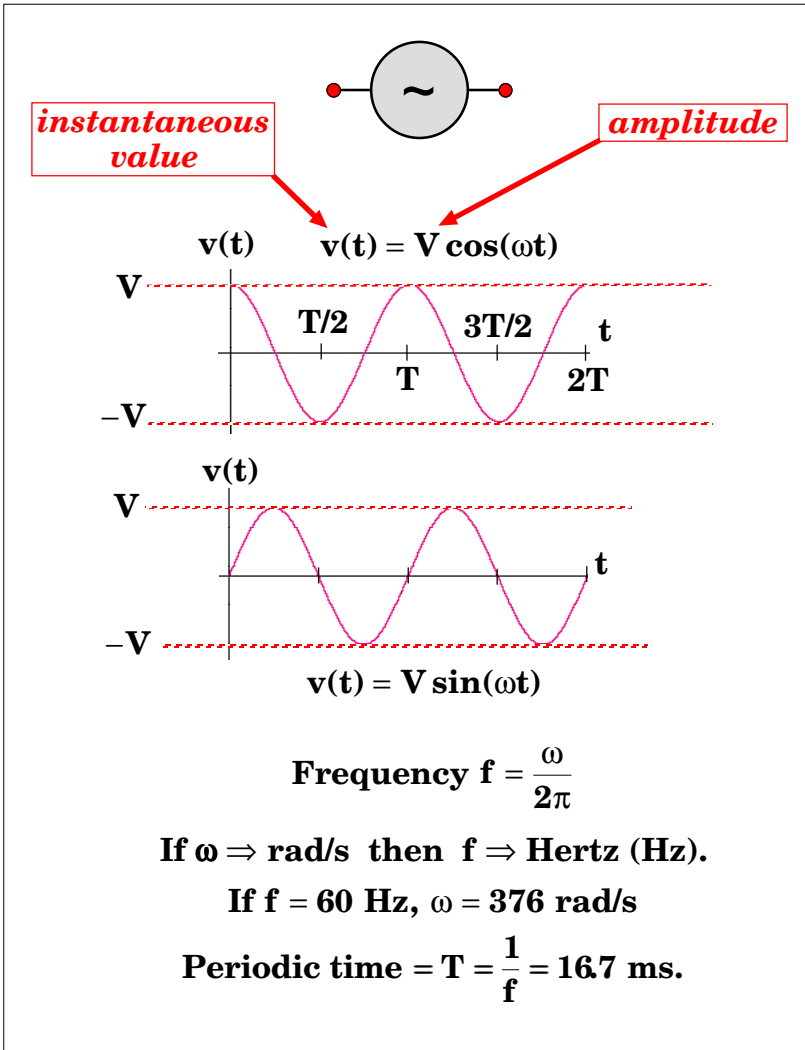
$\epsilon$


$\Phi$

$t$

$T$


Time for one revolution



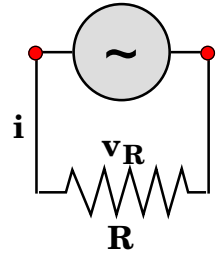

**Instantaneous** current:  $i(t) = i = I \cos(\omega t)$

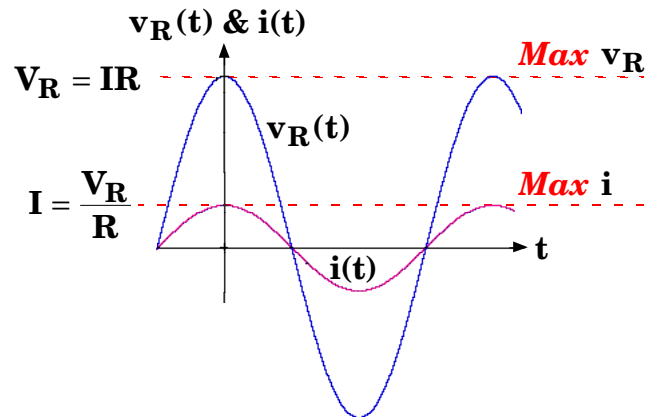
**Instantaneous** potential difference across R:  
 $v_R = iR = IR \cos(\omega t) = V_R \cos(\omega t)$   
 (which is the same as the emf of the generator)



The p.d. and current are **in-phase**.

$$i = I \cos(\omega t)$$
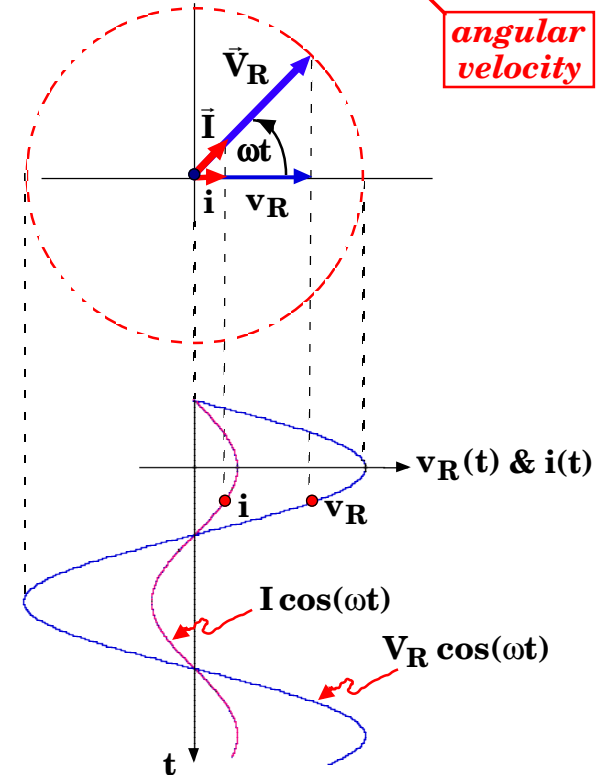
$$v_R = IR \cos(\omega t) = V_R \cos(\omega t)$$




A “Phasor” is a rotating vector. They can be added just like ordinary vectors.

Power dissipated in a resistor:

The *instantaneous* power  $p_R = v_R i$ .

But  $i = I \cos(\omega t)$  and  $v_R = IR \cos(\omega t)$
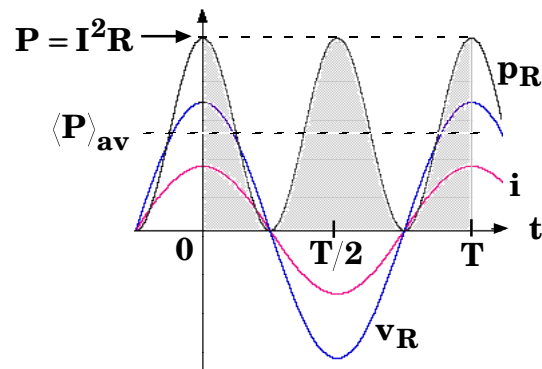
$$\therefore p_R = I^2 R \cos^2(\omega t)$$




The *average power* (over one period):

$$\langle P \rangle_{av} = \frac{\text{Energy dissipated in one period}}{\text{time of one period}}$$

$$= \frac{1}{T} \int_0^T I^2 R \cos^2(\omega t) dt = \frac{1}{2} I^2 R$$

i.e., *half the maximum power*.

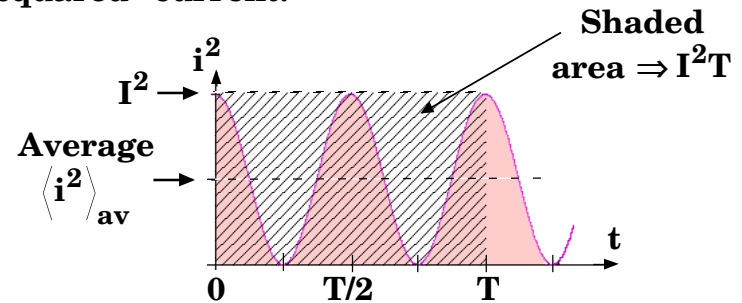Let's look for a moment at  $i^2 = I^2 \cos^2(\omega t)$ , the "squared" current.



Average "squared" current over one cycle is:

$$\langle i^2 \rangle_{av} = \frac{1}{T} \int_0^T I^2 \cos^2(\omega t) dt = \frac{1}{2} I^2.$$

Define *the root mean square (rms)* current as:


$$I_{rms} = \sqrt{\langle i^2 \rangle_{av}} = \sqrt{\frac{1}{2} I^2} = \frac{I}{\sqrt{2}} (= 0.707I)$$

$$\dots \text{ and similarly: } V_{rms} = \frac{V}{\sqrt{2}} (= 0.707V).$$

From before, average power:  $\langle P \rangle_{av} = \frac{1}{2} I^2 R$

$$= I_{rms}^2 R \quad (= V_{rms} I_{rms} = \frac{V_{rms}^2}{R})$$

**Problem 29.23 page 963:**

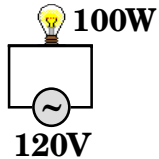

Given :  $\langle P \rangle_{av} = 100W$   
and  $V_{rms} = 120V$ .

But  $\langle P \rangle_{av} = V_{rms} I_{rms}$

$$\therefore I_{rms} = \frac{100}{120} = 0.833A.$$

Also  $I_{rms} = \frac{I_{max}}{\sqrt{2}}$  and  $V_{rms} = \frac{V_{max}}{\sqrt{2}}$


$$\therefore I_{max} = \sqrt{2} \times I_{rms} = 1.18A$$

and  $V_{max} = \sqrt{2} \times V_{rms} = 169.7V$ .


The *maximum* (instantaneous) power is:

$$P_{max} = I_{max} V_{max} = 1.18 \times 169.7 = 200W,$$

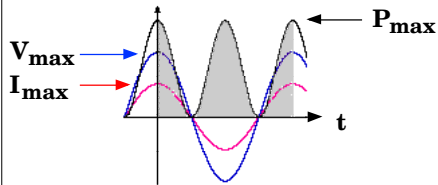i.e., *maximum power = twice average power.*



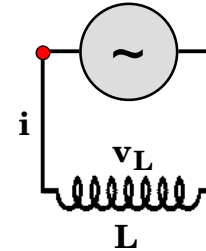Note: the power pulses occur at  $2\omega$ .



**Instantaneous** current:  $i = I \cos(\omega t)$

**Instantaneous** p.d. across inductor:

$$v_L = L \frac{di}{dt} = -I\omega L \sin(\omega t)$$

(which is the same as the emf of the generator.)

But  $-\sin(\omega t) = \cos(\omega t + \pi/2)$  ... *check it out!*

$$\therefore v_L = I\omega L \cos(\omega t + \pi/2)$$

$$X_L = \omega L \text{ "reactance" } (\Omega) \quad \text{"phase angle"}$$

Reactance ( $X_L$ ) is like "ac resistance" but it is not constant; *it depends on frequency.*


$$\text{i.e., } v_L = IX_L \cos(\omega t + \pi/2)$$

Therefore, in terms of angle,  $v_L$  is  $90^\circ$  *ahead* of the current!


$$i = I \cos(\omega t)$$

$$v_L = I X_L \cos(\omega t + 90^\circ) = V_L \cos(\omega t + 90^\circ)$$
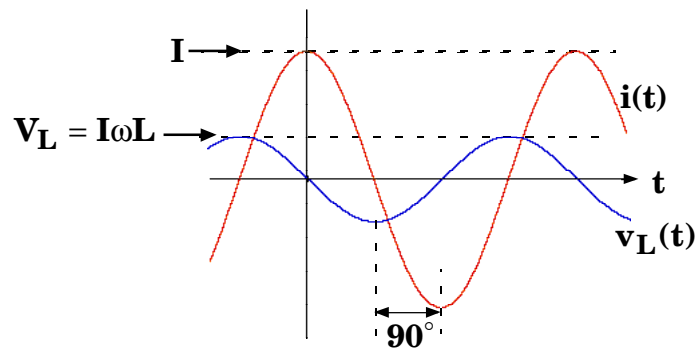
$$\text{i.e., } V_L = I X_L \quad (= I \omega L)$$



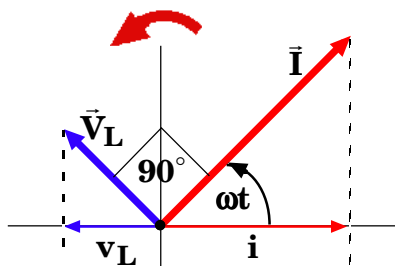$v_L$  is 1/4 of a cycle ( $90^\circ$ ) *ahead* of  $i$




Phasor diagram

**Power in an ideal inductor in an a.c. circuit:**

The *instantaneous* power  $p_L = v_L i$ .

But  $i = I \cos(\omega t)$  and  $v_L = I \omega L \cos(\omega t + 90^\circ)$
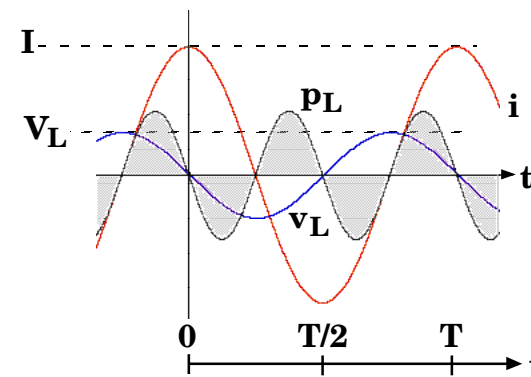
$$\therefore p_L = I^2 \omega L \cos(\omega t) \cos(\omega t + 90^\circ)$$




**The average power (over one cycle):**

$$\langle P \rangle_{\text{av}} = \frac{1}{T} \int_0^T I^2 \omega L \cos(\omega t) \cos(\omega t + 90^\circ) dt = 0.$$

*... You can tell that from the graph! ...*

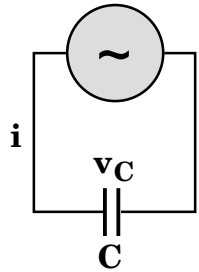**Energy stored in inductor in one quarter-cycle is released in the next quarter-cycle.**



**Instantaneous** current:

$$i = I \cos(\omega t) \left( = \frac{dq}{dt} \right)$$

**Instantaneous** charge on the capacitor:

$$q = \int i \, dt = I \int \cos(\omega t) \, dt = \frac{I}{\omega} \sin(\omega t).$$

$\therefore$  **instantaneous** p.d. across the capacitor is:

$$v_C = \frac{q}{C} = \frac{I}{\omega C} \sin(\omega t),$$

(which is the same as the emf of the generator.)

But  $\sin(\omega t) = \cos(\omega t - \pi/2)$ ,

so  $v_C = \frac{I}{\omega C} \cos(\omega t - \pi/2)$ .

$$X_C = \frac{1}{\omega C} \text{ reactance } (\Omega) \quad \text{phase angle}$$


i.e.,  $v_C = IX_C \cos(\omega t - \pi/2)$

Therefore, in terms of angle,  $v_C$  is  $90^\circ$  **behind** the current.


$$i = I \cos(\omega t)$$

$$v_C = IX_C \cos(\omega t - \pi/2) = V_C \cos(\omega t - \pi/2)$$
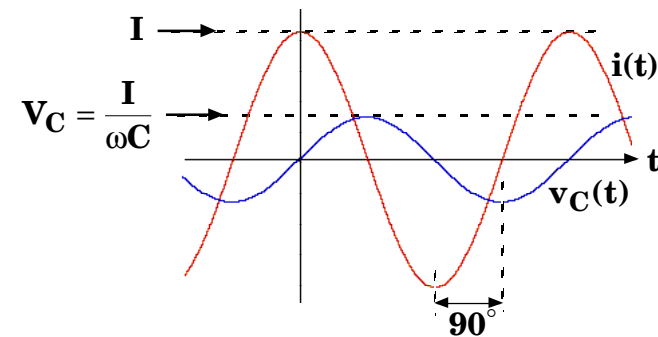
$$\text{i.e., } V_C = IX_C \quad \left( = \frac{I}{\omega C} \right)$$



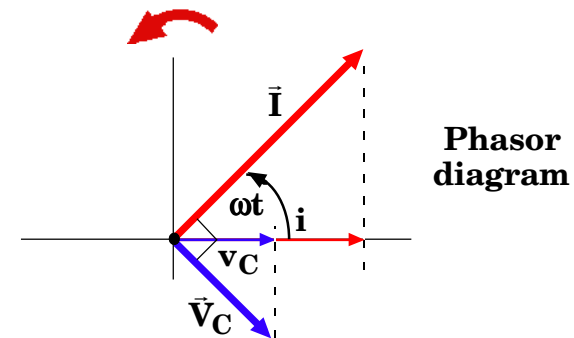$v_C$  is  $1/4$  of a cycle ( $-90^\circ$ ) **behind**  $i$




Phasor diagram

**Power in a capacitor in an a.c. circuit:**

The *instantaneous* power  $p_C = v_C i$ .

But  $i = I \cos(\omega t)$  and  $v_C = \frac{I}{\omega C} \cos(\omega t - 90^\circ)$
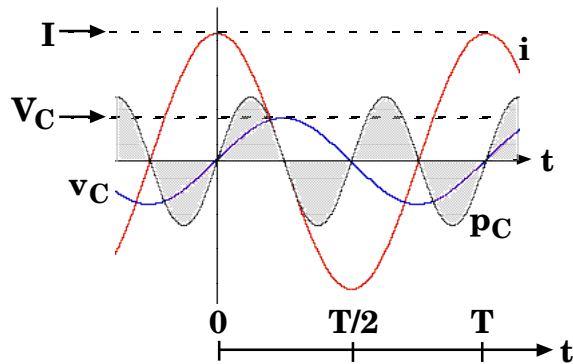
$$\therefore p_C = \frac{I^2}{\omega C} \cos(\omega t) \cos(\omega t - 90^\circ)$$






**The average power (over one cycle):**


$$\langle P \rangle_{av} = \frac{1}{T} \int_0^T \frac{I^2}{\omega C} \cos(\omega t) \cos(\omega t - 90^\circ) dt = 0.$$

*... look at graph!! ...*

**Energy stored in the capacitor in one quarter-cycle is released in the next quarter-cycle.**

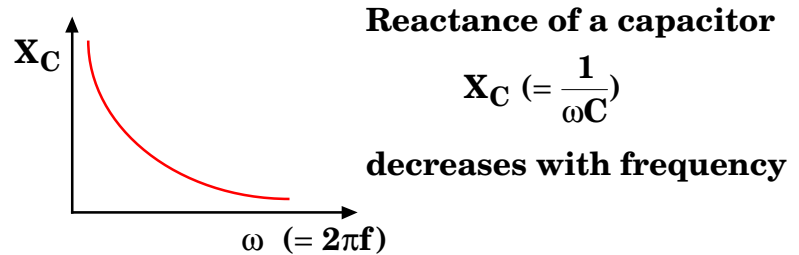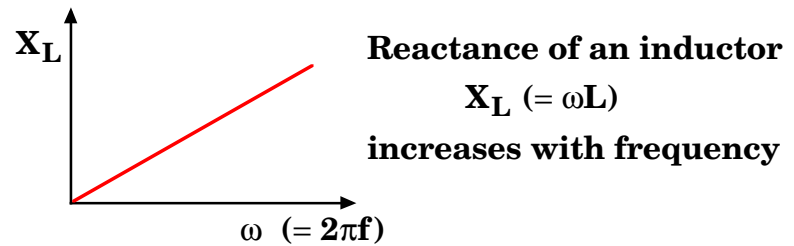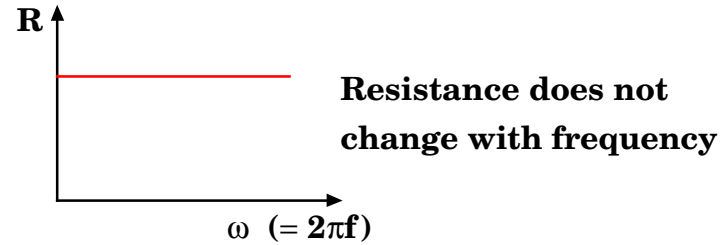
**Comparison of resistance and reactance ...**



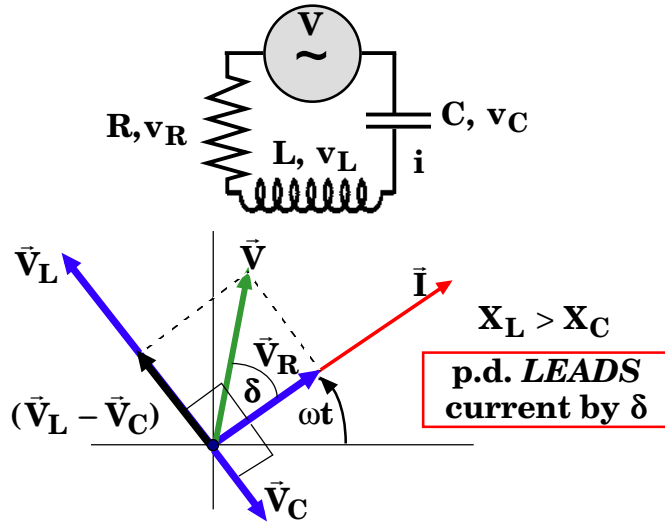


$X_L > X_C$   
**p.d. LEADS**  
**current by  $\delta$**

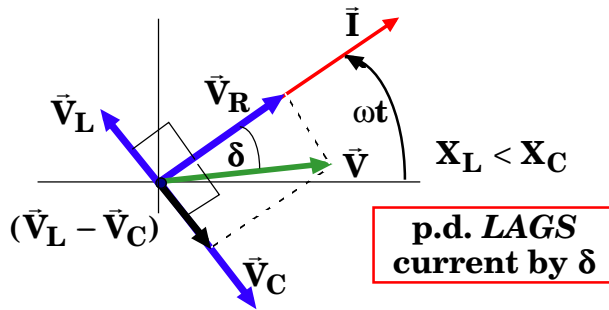By Kirchoff's 2nd rule: **the resultant p.d. supplied the generator**  $\vec{V} = \vec{V}_R + (\vec{V}_L + \vec{V}_C)$ .



$X_L < X_C$   
**p.d. LAGS**  
**current by  $\delta$**

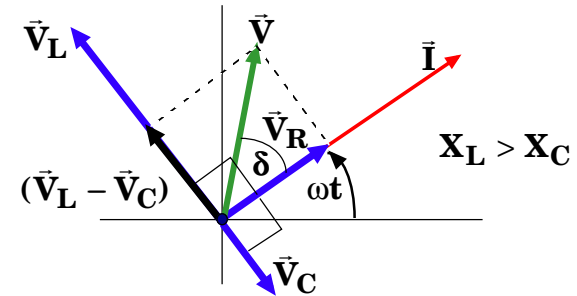The angle  $\delta$  is called the **phase angle**.



$$V = |\vec{V}| = \sqrt{(V_R)^2 + (V_L - V_C)^2}$$

$$= I \sqrt{R^2 + (X_L - X_C)^2} = IZ \Rightarrow \text{"Ohm's law"}$$

where  $Z$  is the **impedance**, given by:

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \Rightarrow \text{(units } \Omega\text{)}.$$


$Z$  is like the "ac resistance" of the circuit. Note:

$Z \Rightarrow Z(\omega)$ . The **instantaneous** p.d. is

$$v = V \cos(\omega t + \delta) = IZ \cos(\omega t + \delta)$$

where  $\delta = \tan^{-1}\left(\frac{V_L - V_C}{V_R}\right) = \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$
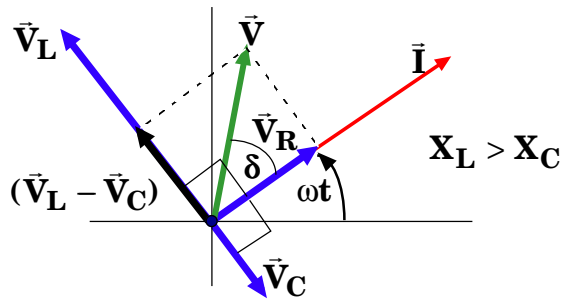
$$= \tan^{-1}\left(\frac{\omega L - 1/\omega C}{R}\right).$$



The *instantaneous* power is:

$$\begin{aligned}
 P &= vi = V\cos(\omega t + \delta) \times I\cos(\omega t) \\
 &= VI\cos^2(\omega t) \cos \delta + \cos(\omega t) \sin(\omega t) \sin \delta \\
 &= VI\cos^2(\omega t) \cos \delta + \frac{1}{2} \sin(2\omega t) \sin \delta
 \end{aligned}$$

If we average over one cycle we have:

$$\langle \cos^2(\omega t) \rangle_{av} = \frac{1}{2} : \langle \sin(2\omega t) \rangle_{av} = 0$$


(so second term  $\Rightarrow 0$ )

$$\therefore \langle P \rangle_{av} = \frac{1}{2} VI \cos \delta$$

$$= V_{rms} I_{rms} \cos \delta$$

*power factor*

In summary ...

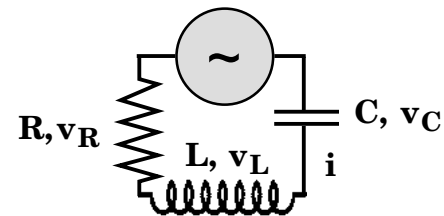

The amplitude of the potential difference across generator (emf) is:

$$V = IZ$$

where  $V$  is the magnitude of the phasor:

$$\vec{V} = \vec{V}_R + \vec{V}_L + \vec{V}_C$$

(not an algebraic sum!) and  $Z$  is the impedance, given by:

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

So, we have relationships between  $V$ ,  $I$  and  $Z$ :

$$V = IZ \quad I = \frac{V}{Z} \quad \text{and} \quad Z = \frac{V}{I}$$

... that are the "*a.c. equivalent*" of Ohm's law.


Since 
$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2},$$

then  $Z$  is a **minimum** at some  $\omega = \omega_0$  when

$$\omega_0 L = \frac{1}{\omega_0 C},$$

i.e., when  $X_L = X_C$ .

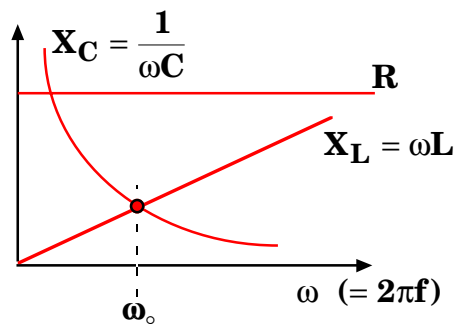Then  $\omega_0 = \sqrt{\frac{1}{LC}} \Rightarrow$  **resonant frequency**.



At resonance,  $\omega = \omega_0$ ,

$$\therefore Z = R,$$

i.e., the impedance is purely **resistive**.

**Problem 29-66 page 966:**

Given :  $L = 1\mu\text{H}$  :  $f_1 = 500\text{kHz}$  :  $f_2 = 1600\text{kHz}$ .

At resonance:  $\omega_0 L = \frac{1}{\omega_0 C}$ .  $\therefore C = \frac{1}{\omega_0^2 L}$

But  $\omega_1 = 2\pi f_1$  and  $\omega_2 = 2\pi f_2$ , so

$$C_1 = \frac{1}{(2\pi \times 500 \times 10^3)^2 \times 1 \times 10^{-6}}$$


$$= 101 \times 10^{-9} \text{F} = 101 \text{nF},$$

and

$$C_2 = \frac{1}{(2\pi \times 1600 \times 10^3)^2 \times 1 \times 10^{-6}}$$

$$= 9.89 \times 10^{-9} \text{F} = 9.89 \text{nF}.$$

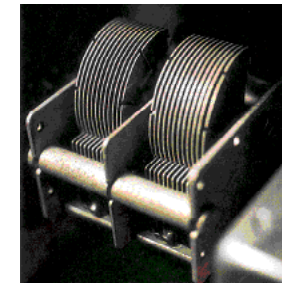Note that the result does not depend on  $R$ .




Variable capacitor

**What's the power factor and the average power at resonance?**

We know:  $\langle P \rangle_{av} = V_{rms} I_{rms} \cos \delta$   
*power factor*

where  $\delta$  is phase angle between current and p.d.  
 But, at resonance,  $\delta = 0$ , i.e., the current and p.d. are in-phase, since  $X_L = X_C$ .

$\therefore \cos \delta = 1.$

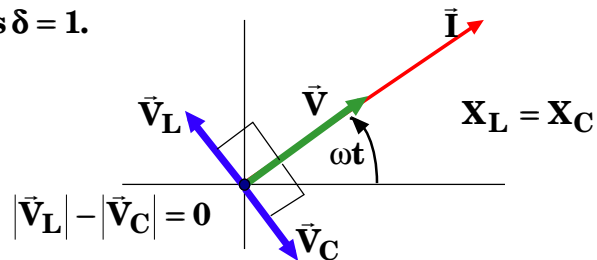


So,  $\langle P(\omega_0) \rangle_{av} = V_{rms} I_{rms}$ , i.e., a maximum.

Also, at resonance:  $V_{rms} = I_{rms} R.$

$\therefore \langle P(\omega_0) \rangle_{av} = V_{rms}^2 / R = I_{rms}^2 R.$

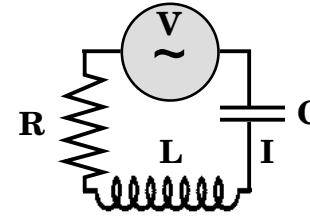**How does the current vary with frequency? Take a generator with a constant voltage amplitude.**



We have: 
$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$


$$= \frac{V}{\sqrt{R^2 + L^2 \left(\omega - \frac{1}{\omega LC}\right)^2}} = \frac{V}{\sqrt{R^2 + L^2 \left(\omega - \frac{\omega_0^2}{\omega}\right)^2}}$$
 i.e., 
$$I = \frac{V\omega}{\sqrt{\omega^2 R^2 + L^2 (\omega^2 - \omega_0^2)^2}}$$

Note, when  $\omega = \omega_0$ ,  $I = \frac{V}{R} \Rightarrow$  *pure resistance*

i.e., at resonance, the current is determined only by  $R$  (and it's a maximum).

What does this function look like?
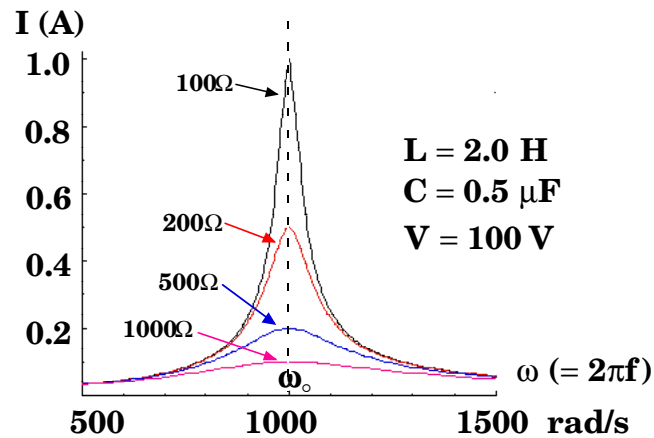
$$I = \frac{V\omega}{\sqrt{\omega^2 R^2 + L^2(\omega^2 - \omega_0^2)^2}}$$



$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{2.0 \times 0.5 \times 10^{-6}}} = 1000 \text{ rad/s,}$$

and independent of R.


$$\therefore f = \frac{\omega_0}{2\pi} = 159.2 \text{ Hz.}$$

Note:  $I_{\max} = \frac{V}{R}$ , when  $\omega = \omega_0$ .

How does the power vary with frequency?

$$\langle P \rangle_{\text{av}} = I_{\text{rms}}^2 R = \frac{V_{\text{rms}}^2 \omega^2 R}{\omega^2 R^2 + L^2(\omega^2 - \omega_0^2)^2}$$

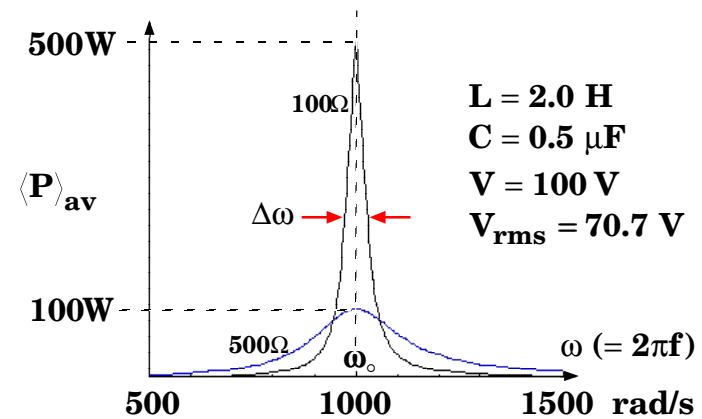Peak power:  $P_{\text{av}}(\omega = \omega_0) \Rightarrow V_{\text{rms}}^2 / R$



Q-value of the circuit ...


$$Q = \frac{\omega_0 L}{R} \approx \frac{\omega_0}{\Delta\omega} = \frac{f_0}{\Delta f}$$

where  $\Delta\omega$  ( $\Delta f$ ) is the width of the peak at half-maximum.

Larger Q  $\Rightarrow$  sharper peak.

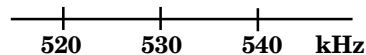
**DISCUSSION PROBLEM [29.1] :**

The frequency difference between radio stations on the AM band is 10kHz. What are suitable Q values at the lowest AM frequency (500kHz) and the highest AM frequency (1600kHz)?



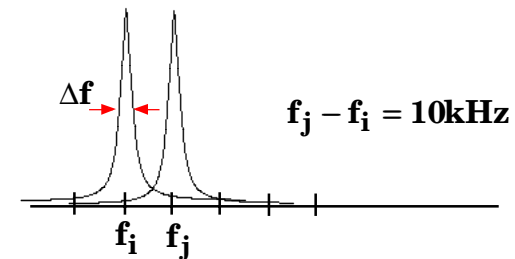**DISCUSSION PROBLEM [29.1] : ...solution ...**

The power curves for the two neighboring stations ( $f_i$  and  $f_j$ ) should be well separated ...



... so that only one of them is “detected”. Make the width of the power functions ( $\Delta f$ ) about 1/5 th (i.e., 20%) of the channel separation,

i.e.,  $\Delta f \sim 0.2(f_j - f_i) = 2\text{kHz}$ .

∴ At the low frequency end:

$$Q = \frac{f}{\Delta f} = \frac{500\text{kHz}}{2\text{kHz}} = 250.$$

∴ At the high frequency end:

$$Q = \frac{f}{\Delta f} = \frac{1600\text{kHz}}{2\text{kHz}} = 800.$$

Therefore, we need a Q value  $> 800$ .

**Problem 29-87 page 967:**

$$I_{\text{rms}} = 10.0\text{A}; \langle P \rangle_{\text{av}} = 720\text{W}; V_{\text{rms}} = 120\text{V}.$$

(a) By definition:  $V = IZ$  i.e.,  $V_{\text{rms}} = I_{\text{rms}}Z$ .

$$\therefore Z = V_{\text{rms}}/I_{\text{rms}} = 120/10 = 120\Omega.$$

(b) Also,  $\langle P \rangle_{\text{av}} = I_{\text{rms}}^2 R$  ... *why only R??*

where  $R$  is the resistance of the “device”.

$$\therefore R = \langle P \rangle_{\text{av}} / I_{\text{rms}}^2 = 7.20\Omega.$$


From notes we have:  $Z = \sqrt{R^2 + (X_L - X_C)^2}$ ,

$$\therefore Z^2 = R^2 + (X_L - X_C)^2 \Rightarrow R^2 + X^2,$$

where  $X$  is the reactance of the “device”.

$$\therefore X = \sqrt{Z^2 - R^2} = \sqrt{120^2 - 7.20^2} = 9.60\Omega.$$

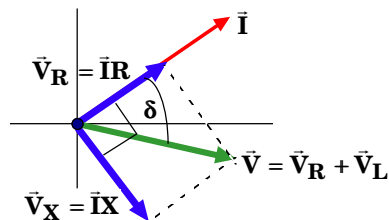(c) If the current *leads* the p.d., the device is a (non-ideal) capacitor.



*Extra ...* from notes:

$$\delta = \tan^{-1}(X/R) = 53.1^\circ$$